

Foundations of Math

Week 4 - Boolean algebra: Logic gates and switching functions

Dr. Titus von der Malsburg

November 6, 2019

Agenda for today

- ▶ Solutions for homework from last week
 - ▶ Exercises 36.1 – 36.16 (submit one .pdf)
- ▶ Homework for next week.

Plan for the rest of the term (tentative):

- ▶ Chapter 1: Standard functions and techniques
- ▶ Chapters 2-4: Differentiation
- ▶ Chapters 14-15: Integration
- ▶ Chapters 7-10: Linear Algebra
- ▶ Chapters 39-40: Probability and statistics

Self-tests

- ▶ It is strongly recommend to do them.
- ▶ A variant usually appears in the exercises.
- ▶ Sometimes they are the key to solving exercises.
- ▶ If you have problems with the self-test, you are not ready to move ahead.

Exercise 36.1:

Read through Example 36.1. Now prove the other absorption law:

$$a * (a \oplus b) = a$$

(Example 36.1 and this result illustrate the duality principle, which states that any theorem which can be proved in Boolean algebra implies another theorem with $*$ and \oplus interchanged for the same elements.)

Idea was not to use laws in box 36.3.

For all $a, b \in B$

$$a * (a \oplus b) = (a \oplus 0) * (a \oplus b) \quad (\text{Identity law})$$

$$= a \oplus (0 * b) \quad (\text{Distributive law})$$

Now

$$0 * b = \bar{b} * b * b \quad (\text{Complement law})$$

$$= \bar{b} * b \quad (\text{Definition of } *)$$

$$= 0 \quad (\text{Complement law})$$

Finally

$$a * (a \oplus b) = a \oplus 0$$

$$= a \quad (\text{Identity law})$$

Exercise 36.2:

(Section 36.1). Prove the de Morgan result

$$\overline{a \oplus b} = \bar{a} * \bar{b},$$

by showing that $(a \oplus b) \oplus (\bar{a} * \bar{b}) = 1$. Explain how the duality result (Problem 36.1) gives the other de Morgan theorem.

First of all:

$$\overline{a \oplus b} = \bar{a} * \bar{b} \qquad \text{(Add } a \oplus b \text{ on both sides.)}$$

$$(a \oplus b) \oplus \overline{a \oplus b} = (a \oplus b) \oplus \bar{a} * \bar{b}$$

$$1 = (a \oplus b) \oplus \bar{a} * \bar{b} \qquad \text{(Complement law)}$$

$$\begin{aligned}
 a \oplus b \oplus \bar{a} * \bar{b} &= b \oplus (a \oplus \bar{a}) * (a \oplus \bar{b}) && \text{(Distr.)} \\
 &= b \oplus (a \oplus \bar{b}) && \text{(Identity)} \\
 &= (b \oplus \bar{b}) \oplus a && \text{(Comm., Assoc.)} \\
 &= 1 \oplus a && \text{(Identity)} \\
 &= 1 && \text{(Identity)}
 \end{aligned}$$

Exercise 36.3:

(Section 36.1). Let B be the Boolean algebra with the two elements 0 and 1. For arbitrary $a, b \in B$, prove the following:

► $a * (\bar{a} \oplus b) = a * b$

$$\begin{aligned} a * (\bar{a} \oplus b) &= (a * \bar{a}) \oplus (a * b) && \text{(Distributive law)} \\ &= 1 \oplus a * b && \text{(Complement law)} \\ &= a * b && \text{(Identity law)} \end{aligned}$$

► $(a \oplus b) * (a \oplus \bar{b}) = a$

$$\begin{aligned}(a \oplus b) * (a \oplus \bar{b}) &= a \oplus b * \bar{b} \\ &= a \oplus 0 \\ &= a\end{aligned}$$

► $(a \oplus b) * \bar{a} * \bar{b} = 0$

$$\begin{aligned}(a \oplus b) * \bar{a} * \bar{b} &= (\bar{a} * a \oplus \bar{a} * b) * \bar{b} \\ &= \bar{a} * b * \bar{b} \\ &= \bar{a} * 0 \\ &= 0\end{aligned}$$

Exercise 36.4:

(Section 36.1). Using the laws of Boolean algebra for the set with two elements 0 and 1, show that:

► $a * b \oplus a * \bar{b} = a$

► $a \oplus \bar{a} * \bar{b} * c = a \oplus \bar{b} * c$

Use the result to obtain the truth tables in each case.

$$\begin{aligned}
 a * b \oplus a * \bar{b} &= a * (b \oplus \bar{b}) \\
 &= a * 1 \\
 &= a
 \end{aligned}$$

Truth table:

a	b	\bar{b}	$a * b$	$a * \bar{b}$	$a * b \oplus a * \bar{b}$
0	0	1	0	0	0
0	1	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1

$$\begin{aligned}
a \oplus \bar{a} * \bar{b} * c &= a \oplus (\bar{a} * \bar{b} * c) \\
&= (a \oplus \bar{a}) * (a \oplus \bar{b}) * (a \oplus c) \\
&= (a \oplus \bar{b}) * (a \oplus c) \\
&= a \oplus (\bar{b} * c) \\
&= a \oplus \bar{b} * c
\end{aligned}$$

How do we know that the distributive generalizes to products with more than two factors?

Truth table:

a	b	c	$\bar{b} * c$	$a \oplus \bar{b} * c$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

Exercise 36.5:

(Section 36.4). In Problem 36.4b, it is shown that

$$a \oplus \bar{a} * \bar{b} * c = a \oplus \bar{b} * c.$$

Design two sequences of gates which give the same output for the inputs a , b , and c . The resultant gates are said to be logically equivalent.

Exercise 36.6:

(Section 36.4). Design a circuit of gates to produce the output

$$(a \oplus \overline{b}) * (a \oplus \overline{c}).$$

Construct the truth table for this Boolean expression.

Exercise 36.7:

(Section 36.1). Show that the Boolean expression $(a \oplus b) * (\bar{a} \oplus b) \oplus a$ and $a \oplus b$ are equivalent.

$$\begin{aligned}(a \oplus b) * (\bar{a} \oplus b) \oplus a &= (a \oplus a \oplus b) * (a \oplus \bar{a} \oplus b) \\&= (a \oplus b) * (a \oplus \bar{a} \oplus b) \\&= (a \oplus b) * (1 \oplus b) \\&= (a \oplus b) * 1 \\&= a \oplus b\end{aligned}$$

Exercise 36.8:

(Section 36.1). Show that the following Boolean expressions are equivalent:

- ▶ $a \oplus b$
- ▶ $a \oplus b * b$

$$\begin{aligned} a \oplus b * b &= a \oplus (b * b) \\ &= a \oplus b \end{aligned}$$

But how do we know that $b * b = b$?

- ▶ b could be 1, then $b * 1 = b$.
- ▶ b could be 0, then $b * 0 = 0 = b$.

Exercise 36.9:

(Section 36.3). Find a Boolean expression f which corresponds to the truth table shown in Table 36.13.


a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$(\bar{a} * \bar{b}) \oplus (a * \bar{b}) = (\bar{a} \oplus a) * \bar{b} = \bar{b}$$

Exercise 36.10:


(Section 36.3). Construct Boolean expression for the output f in the devices shown in Figs. 36.17a–d. Construct the truth tables in each case.

(a)

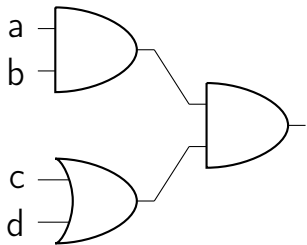


► $a * b * (c \oplus d)$

(b)

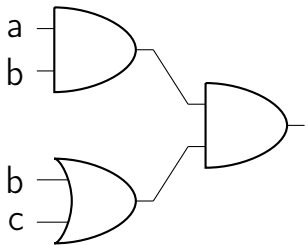


► $a * b * (b \oplus c) = a * b$

(c)

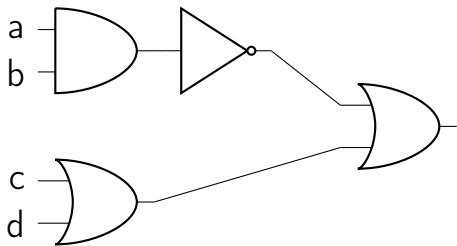

► $\overline{a * b} \oplus (c \oplus d) = \bar{a} \oplus \bar{b} \oplus c \oplus d$

(d)

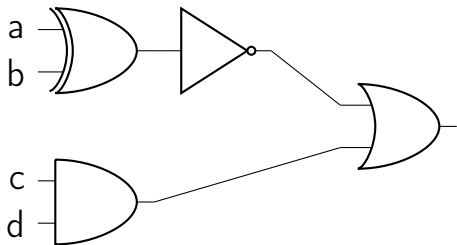

► $\overline{\overline{a} * b \oplus a * \overline{b} \oplus c * d} = a * b \oplus \overline{a} * \overline{b} \oplus c * d$

Exercise 36.11:

Find the output f and g in the logic circuits shown in Fig. 36.18. This device can represent binary addition in which g is the 'carry' in the binary table shown in Table 36.14. The output g gives the '1' in the '10' in the binary sum $1 + 1 = 10$.

► $g = a * b$

► $f = \overline{a * b} * (a \oplus b)$

$x = a$	$y = b$	$x + y$	g	f
0	0	0	0	0
0	1	1	0	1
1	0	1	0	1
1	1	10	1	0

Exercise 36.12:

(Section 36.3). Reproduce the logic gate in Fig. 36.6 using just the NOR gate. (Circuit is $a * b \oplus c \oplus d$).

We need to build $*$ and \oplus using just NOR (\downarrow):

► $a * b = \overline{a} \downarrow \overline{b}$

► $\overline{a} = a \downarrow a$

► Therefore: $a * b = (a \downarrow a) \downarrow (b \downarrow b)$

► $a \oplus b = \overline{a \downarrow b} = (a \downarrow b) \downarrow (a \downarrow b)$

► All taken together:

$$\begin{aligned} a * b \oplus c \oplus d &= (((a \downarrow a) \downarrow (b \downarrow b)) \downarrow ((c \downarrow d) \downarrow (c \downarrow d))) \downarrow \\ &\quad (((a \downarrow a) \downarrow (b \downarrow b)) \downarrow ((c \downarrow d) \downarrow (c \downarrow d))) \\ &= (a \downarrow c \downarrow d) \downarrow (b \downarrow c \downarrow d) \end{aligned}$$

Scratchpad:

Exercise 36.13:

(Section 36.4). Using the disjunctive normal form, construct a Boolean expression f for the truth tables given in Tables 36.15 and 36.16.

Table: 36.15

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1

$$f = \bar{a} * b \oplus$$

$$a * \bar{b} \oplus$$

$$a * b = a \oplus b$$

Table: 36.16

a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$f = \bar{a} * \bar{b} * \bar{c} \oplus$$

$$\bar{a} * b * c \oplus$$

$$a * \bar{b} * \bar{c} \oplus$$

$$a * b * \bar{c}$$

Exercise 36.14:

(Section 36.3). Show that any Boolean expression can be modelled using just a NAND gate. (Hint: use a method similar to that explained in Example 36.4.)

a	b	$a \uparrow b$	\bar{a}	$a * b$	$a \oplus b$
0	0	1	1	0	0
0	1	1	1	0	1
1	0	1	0	0	1
1	1	0	0	1	1

We have to show that $*$ (conjunction), \oplus (disjunction), and \bar{a} (negation) can be expressed in terms of just NAND:

- ▶ $\bar{a} = a \uparrow a$
- ▶ $a * b = \overline{a \uparrow b} = (a \uparrow b) \uparrow (a \uparrow b)$
- ▶ $a \oplus b = \bar{a} \uparrow \bar{b} = (a \uparrow a) \uparrow (b \uparrow b)$

Exercise 36.15:

(Section 36.4). Find switching functions for the switching circuits shown in Figs 36.19a,b.

1. $a_1 \oplus a_2 \oplus ((a_3 \oplus a_4) * a_5)$

2. $a_1 \oplus ((a_2 * a_3 \oplus a_4) * a_5)$

Exercise 36.16:

A lecture theatre has three entrances and the lighting can be controlled from each entrance; that is, it can be switched on or off independently. The light is 'on' if the output f equals 1 and 'off' if $f = 0$. Let $a_i = 1$ ($i = 1, 2, 3$) when switch i is up, and let $a_i = 0$ ($i = 1, 2, 3$) when it is down. Construct a truth table for the state of the lighting for all states of the switches. Also specify a Boolean expression which will control the lighting.

a_1	a_2	a_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$\begin{aligned}f = & (\overline{a_1} * \overline{a_2} * a_3) \oplus \\& (\overline{a_1} * a_2 * \overline{a_3}) \oplus \\& (a_1 * \overline{a_2} * \overline{a_3}) \oplus \\& (a_1 * a_2 * a_3)\end{aligned}$$

Is there another solution?
Yes, the complement, \overline{f} !

Homework for next week

- ▶ Read sections 1.1–1.9 in Chapter 1 (27 pages).
- ▶ Do exercises: 1.1 – 1.14, 1.18, 1.20, 1.21.

End of file.